Lab Activity Blinking LED.docx
File View Tools Help
Open with Google Docs
Page 1 / 3 100%

LABORATORY ACTIVITY 1

Blinking an LED with Arduino UNO Using a Series-Connected 1 k

Name: _____

Section / Grade Level: _____

Date: _____

Instructor: _____

I. Learning Outcomes

At the end of this activity, the trainee/student should be able to:

- Identify and correctly connect the components of a simple LED circuit on a breadboard.
- Explain the purpose of a current-limiting resistor in an LED circuit.
- Write and upload a basic Arduino sketch to control a digital output pin.
- Demonstrate the operation of the blinking LED circuit and troubleshoot common wiring or

II. Materials and Equipment

Qty	Item / Component	Specification / Notes
1	Arduino UNO board	With USB cable
1	Breadboard	Half-size or full-size
1	LED	Any color, 5mm stand
1	Resistor	1 kΩ (brown-black-red
2	Jumper wires	Male-to-male, one for
1	Computer	With Arduino IDE inst

III. Circuit Diagram

Study the reference circuit diagram below before assembling your own on the breadboard.

